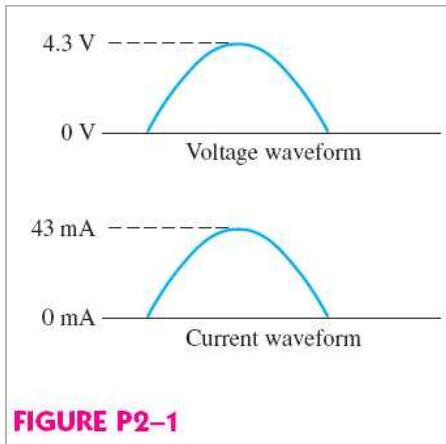


## Chapter 2

1. See Figure P2-1.



**FIGURE P2-1**

$$2. \text{ primary side : } V_{pk} = 115\sqrt{2} V = 162.6 V$$

$$\text{secondary side : } V_{pk} = \frac{162.6 V}{2} = 81.3 V$$

Peak voltage delivered to the load

$$= V_{L(pk)} = 81.3 V - 0.7 V = 80.6 V$$

Peak power delivered to the load

$$= \frac{V_L^2}{R_L} = \frac{(80.6 V)^2}{220 \Omega} = 29.5 W$$


3. (a) Full-wave rectifier (전파 정류기)

$$(b) V_{p(sec)} = \left( \frac{N_{sec}}{N_{pri}} \right) V_{p(\in)} = (0.25)(1.414)(80 V) = 28.3 V$$

$$(c) V_{\frac{1}{2}sec} = \frac{V_{p(sec)}}{2} = \frac{28.3 V}{2} = 14.2 V$$

(reference is center tap)

(d) See Figure P2-3.

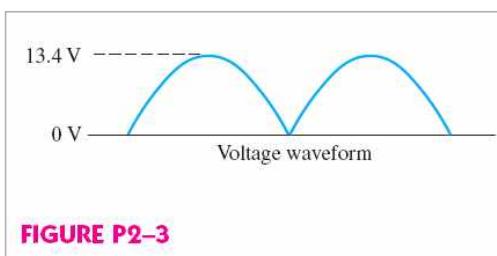


**FIGURE P2-3**

$$(e) I_{p(diode)} = I_{p(R_L)} = \frac{14.2 V - 0.7 V}{1 k\Omega} = 13.5 mA$$

$$(f) PIV = V_{p(sec)} = 28.3 V$$

4. 그림 P2-4에 도시 된 바와 같이, 다이오드 D1과 D2 역방향으로 설계

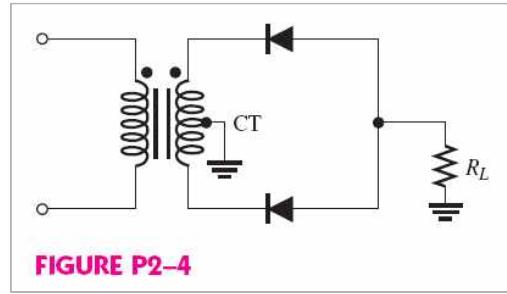

**FIGURE P2-4**

$$5. V_p = 50 V / 0.637 = 78.5 V, PIV = 78.5 V (\text{평균값으로})$$

6. Peak voltage (파크 전압 값)

7. 부하정격 :

$$= \left( \frac{V_{out} - V_{FL}}{V_{FL}} \right) 100\% = \left( \frac{15.5 V - 14.9 V}{14.9 V} \right) 100\% = 4\%$$

8.

$$V_{out} = V_{NoLoad} - 0.5\% (V_{NoLoad}) = 12 V - 0.005(12 V) = 11.94 V$$

$$9. V_{\in(MIN)} = (2.0mA)(560\Omega) + 5.0 V = 6.12 V$$

$$V_{\in(MAX)} = (30mA)(560\Omega) + 5.0 V = 21.8 V$$

10. 부하정격

$$= \left( \frac{V_{NL} - V_{FL}}{V_{FL}} \right) 100\% = \left( \frac{8.0 V - 7.8 V}{7.8 V} \right) 100\% = 2.6\%$$

11. 교재 Page511 참조

- |               |             |
|---------------|-------------|
| 12.(a) 작동 제대로 | (b) 다이오드 개방 |
| (c) 제대로 작동    | (d) 다이오드 개방 |

13.

$$V_{out} = 5.0 V = 1.25 V \left( \frac{R_1 + R_2}{R_1} \right) = 1.25 V \left( \frac{240\Omega + R_2}{240\Omega} \right)$$

$$5.0 V = 1.25 V + \left( \frac{1.25 V}{240\Omega} \right) R_2, \quad R_2 = 3.75 V \left( \frac{240\Omega}{1.25 V} \right) = 720\Omega$$

14.

$$V_{out} = 1.25 V \left( \frac{R_1 + R_2}{R_1} \right) = 1.25 \left( \frac{240\Omega + 1500\Omega}{240\Omega} \right) = 9.06 V$$

15. 교재 Page511 참조